

Laboratory Report # 4

Name: Paul Emmanuel G. Corsino

Date Completed: 10/5/2023

Laboratory Exercise Title: Dataflow Modeling of Combinational Circuits

Target Course Outcomes:

CO1: Create descriptions of digital hardware components such as in combinational and sequential circuits using synthesizable Verilog HDL constructs.


CO2: Verify the functionality of HDL-based components through design verification tools.

Exercise 4A: 4-Bit Comparator

Exercise 4A: 4-Bit Comparator

- Proof of successful design synthesis (*screenshot showing 0 errors*)
- Proof of successful simulation results with required number of test cases (*screenshots of simulation results with annotations or discussion of results*)

Figure 1.0 – Flow Summary

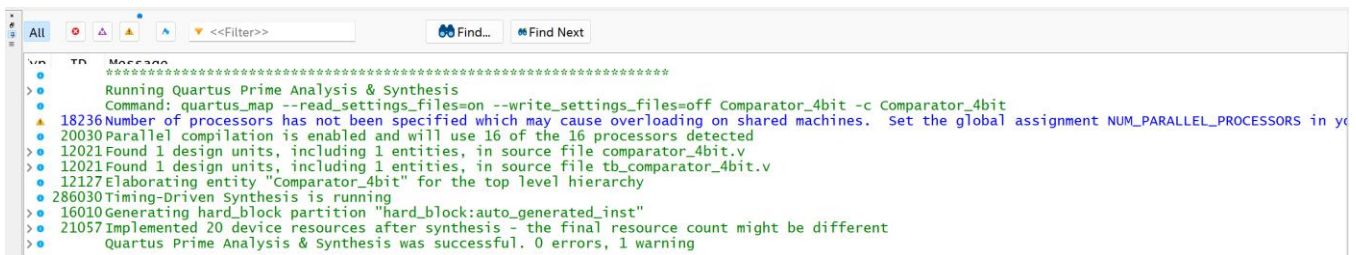

```

*****
Running Quartus Prime Analysis & Synthesis
Command: quartus_map --read_settings_files=on --write_settings_files=off Comparator_4bit -c Comparator_4bit
18236Number of processors has not been specified which may cause overloading on shared machines. Set the global assignment NUM_PARALLEL_PROCESSORS in y
20030Parallel compilation is enabled and will use 16 of the 16 processors detected
12021Found 1 design units, including 1 entities, in source file comparator_4bit.v
12021Found 1 design units, including 1 entities, in source file tb_comparator_4bit.v
12127Elaborating entity "Comparator_4bit" for the top level hierarchy
28603Timing-Driven Synthesis is running
16010Generating hard_block partition "hard_block:auto_generated_inst"
21057Implemented 20 device resources after synthesis - the final resource count might be different
Quartus Prime Analysis & Synthesis was successful. 0 errors, 1 warning
  
```

Figure 1.1 - Proof of successful design synthesis

 


Figure 1.2– 4-Bit Comparator RTL Simulation Output (Waveform)



```
# == Test Bench of 4-Bit Comparator ==  
# A < B  
# Time = 0 ns A = 1 | [0001] B = 8 [1000] R = 001  
# Time = 10 ns A = 2 | [0010] B = 9 [1001] R = 001  
# Time = 20 ns A = 3 | [0011] B = 10 [1010] R = 001  
# Time = 30 ns A = 4 | [0100] B = 11 [1011] R = 001  
# A == B  
# Time = 40 ns A = 0 | [0000] B = 0 [0000] R = 010  
# Time = 50 ns A = 10 | [1010] B = 10 [1010] R = 010  
# Time = 60 ns A = 9 | [1001] B = 9 [1001] R = 010  
# Time = 70 ns A = 15 | [1111] B = 15 [1111] R = 010  
# A > B  
# Time = 80 ns A = 8 | [1000] B = 0 [0000] R = 100  
# Time = 90 ns A = 15 | [1111] B = 7 [0111] R = 100  
# Time = 100 ns A = 6 | [0110] B = 5 [0101] R = 100  
# Time = 110 ns A = 12 | [1100] B = 3 [0011] R = 100  
# ** Note: $stop : C:/School/HDL/Comparator_4bit/tb_Comparator_4bit.v(42)  
# Time: 120 ns Iteration: 0 Instance: /tb_Comparator_4bit  
# Break in Module tb_Comparator_4bit at C:/School/HDL/Comparator_4bit/tb_Comparator_4bit.v line 42
```

Figure 1.3 – 4-Bit Comparator Testbench Monitor Output

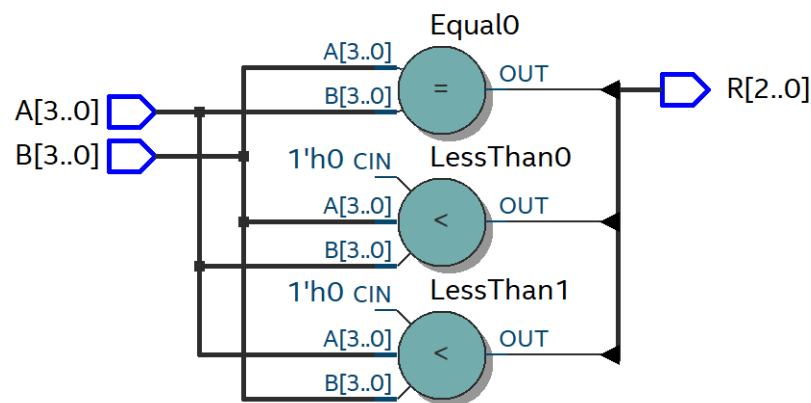


Figure 1.4 – 4-Bit Comparator RTL Viewer

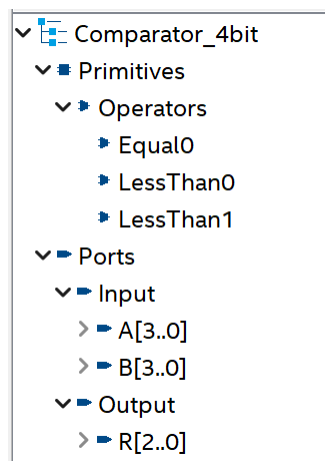


Figure 1.5 – I/O Ports



Exercise 4B: n-Bit 4-to-1 Line Multiplexer (Part 1: 4-Bit 4x1 Line Multiplexer)

Exercise 4B: n-Bit 4-to-1 Line Multiplexer (Part 1 and Part 2)

- Proof of successful design synthesis (screenshot showing 0 errors)
- Proof of successful simulation results with required number of test cases (screenshots of simulation results with annotations or discussion of results)

Figure 2.0 – Flow Summary

```

*****
> Running Quartus Prime Analysis & Synthesis
> Command: quartus_map --read_settings_files=on --write_settings_files=off Mux_4x1_nbit -c Mux_4x1_nbit
> 18236 Number of processors has not been specified which may cause overloading on shared machines. Set the global assignment NUM_PARALLEL_PROCESSORS in y
> 20030 Parallel compilation is enabled and will use 16 of the 16 processors detected
> 12021 Found 1 design units, including 1 entities, in source file mux_4x1_nbit.v
> 12021 Found 1 design units, including 1 entities, in source file tb_mux_4x1_4bit.v
> 12021 Found 1 design units, including 1 entities, in source file tb_mux_4x1_8bit.v
> 12127 Elaborating entity "Mux_4x1_nbit" for the top level hierarchy
> 286030 Timing-Driven Synthesis is running
> 16010 Generating hard_block partition "hard_block:auto_generated_inst"
> 21057 Implemented 30 device resources after synthesis - the final resource count might be different
> Quartus Prime Analysis & Synthesis was successful. 0 errors, 1 warning

```

Figure 2.1 – Proof of successful design synthesis

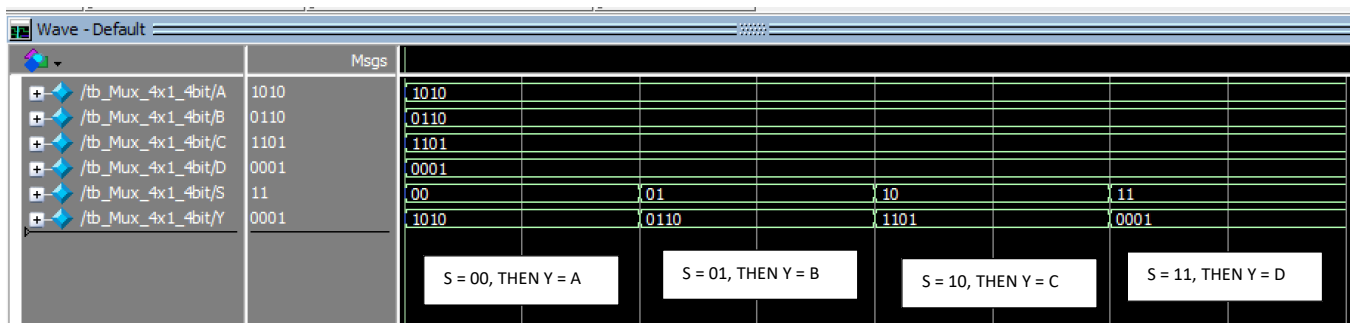


Figure 2.2 - 4-Bit 4x1 Line Multiplexer RTL Simulation Output (Waveform)

```

# == Test Bench of 4-Bit 4x1 Multiplexer ==
# == A ==
# Time = 0 ns | A = 10 [1010] | B = 6 [0110] | C = 13 [1101] | D = 1 [0001] | S = 0 [00] | Y = 10 [1010] |
# == B ==
# Time = 10 ns | A = 10 [1010] | B = 6 [0110] | C = 13 [1101] | D = 1 [0001] | S = 1 [01] | Y = 6 [0110] |
# == C ==
# Time = 20 ns | A = 10 [1010] | B = 6 [0110] | C = 13 [1101] | D = 1 [0001] | S = 2 [10] | Y = 13 [1101] |
# == D ==
# Time = 30 ns | A = 10 [1010] | B = 6 [0110] | C = 13 [1101] | D = 1 [0001] | S = 3 [11] | Y = 1 [0001] |
# ** Note: $stop : C:/School/HDL/Mux_4x1_nbit/tb_Mux_4x1_4bit.v(41)
# Time: 40 ps Iteration: 0 Instance: /tb_Mux_4x1_4bit
# Break in Module tb_Mux_4x1_4bit at C:/School/HDL/Mux_4x1_nbit/tb_Mux_4x1_4bit.v line 41

```

Figure 2.3 – 4-Bit 4x1 Line Multiplexer Testbench Monitor Output

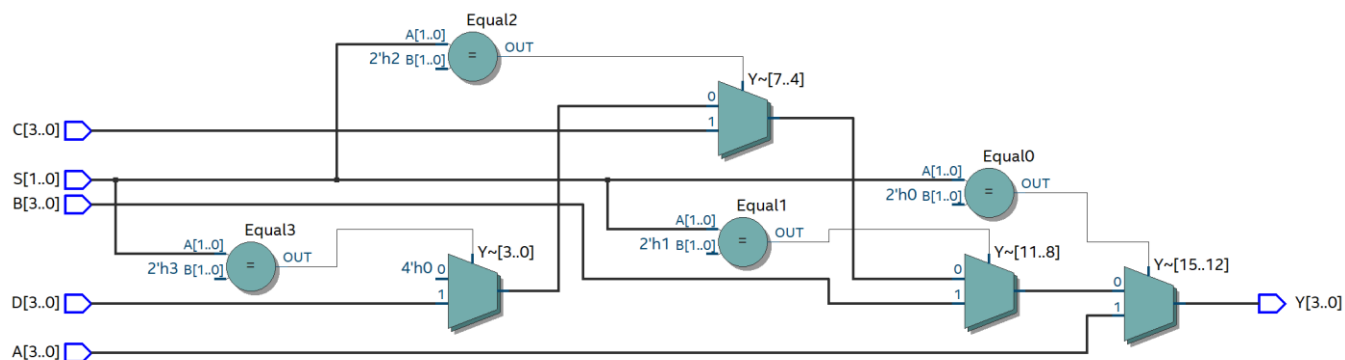


Figure 2.4 – 4-Bit 4x1 Line Multiplexer RTL Viewer

- ▼ Mux_4x1_nbit
 - ▼ Primitives
 - ▼ Logics
 - > Y~[11..8]
 - > Y~[15..12]
 - > Y~[3..0]
 - > Y~[7..4]
 - ▼ Operators
 - Equal0
 - Equal1
 - Equal2
 - Equal3
 - ▼ Ports
 - ▼ Input
 - > A[3..0]
 - > B[3..0]
 - > C[3..0]
 - > D[3..0]
 - > S[1..0]
 - ▼ Output
 - > Y[3..0]

Figure 2.5 – I/O Ports



n-Bit 4-to-1 Line Multiplexer (Part 2: 8-Bit 4x1 Line Multiplexer)

Exercise 4B: n-Bit 4-to-1 Line Multiplexer (Part 1 and Part 2)

- Proof of successful design synthesis (screenshot showing 0 errors)
- Proof of successful simulation results with required number of test cases (screenshots of simulation results with annotations or discussion of results)

Figure 3.0 – Flow Summary

```

*****
Running Quartus Prime Analysis & Synthesis
Command: quartus_map --read_settings_files=on --write_settings_files=off Mux_4x1_nbit -c Mux_4x1_nbit
18236 Number of processors has not been specified which may cause overloading on shared machines. Set the global assignment NUM_PARALLEL_PROCESSORS in y
20030 Parallel compilation is enabled and will use 16 of the 16 processors detected
12021 Found 1 design units, including 1 entities, in source file mux_4x1_nbit.v
12021 Found 1 design units, including 1 entities, in source file tb_mux_4x1_4bit.v
12021 Found 1 design units, including 1 entities, in source file tb_mux_4x1_8bit.v
12127 Elaborating entity "Mux_4x1_nbit" for the top level hierarchy
286030 Timing-Driven Synthesis is running
16010 Generating hard_block partition "hard_block:auto_generated_inst"
21057 Implemented 30 device resources after synthesis - the final resource count might be different
Quartus Prime Analysis & Synthesis was successful. 0 errors, 1 warning

```

Figure 3.1 – Proof of successful design synthesis

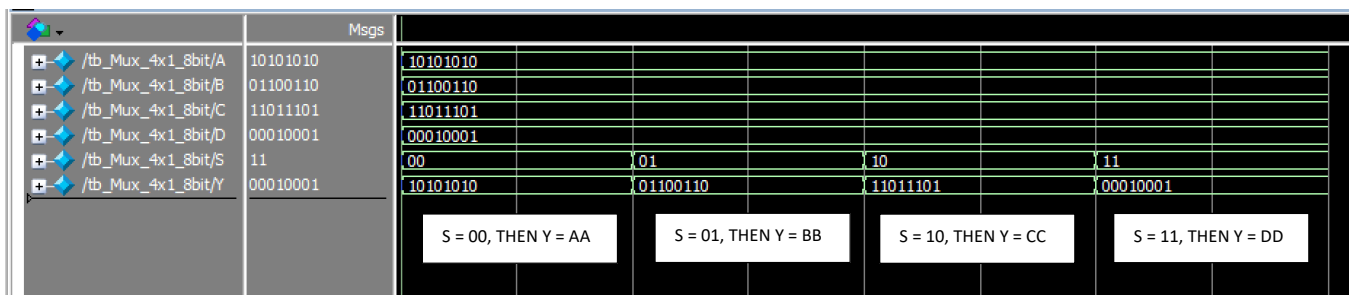


Figure 3.2 – 8-Bit 4x1 Line Multiplexer RTL Simulation Output (Waveform)

```

# == Test Bench of 8-Bit 4x1 Multiplexer ==
# == A ==
# Time = 0 ns | A = 170 [10101010] | B = 102 [01100110] | C = 221 [11011101] | D = 17 [00010001] | S = 0 [00] | Y = 170 [10101010]
# == B ==
# Time = 10 ns | A = 170 [10101010] | B = 102 [01100110] | C = 221 [11011101] | D = 17 [00010001] | S = 1 [01] | Y = 102 [01100110]
# == C ==
# Time = 20 ns | A = 170 [10101010] | B = 102 [01100110] | C = 221 [11011101] | D = 17 [00010001] | S = 2 [10] | Y = 221 [11011101]
# == D ==
# Time = 30 ns | A = 170 [10101010] | B = 102 [01100110] | C = 221 [11011101] | D = 17 [00010001] | S = 3 [11] | Y = 17 [00010001]
# ** Note: $stop : C:/School/HDL/Mux_4x1_nbit/tb_Mux_4x1_8bit.v(41)
# Time: 40 ps Iteration: 0 Instance: /tb_Mux_4x1_8bit
# Break in Module tb_Mux_4x1_8bit at C:/School/HDL/Mux_4x1_nbit/tb_Mux_4x1_8bit.v line 41

```

Figure 3.3 – 8-Bit 4x1 Line Multiplexer Testbench Monitor Output

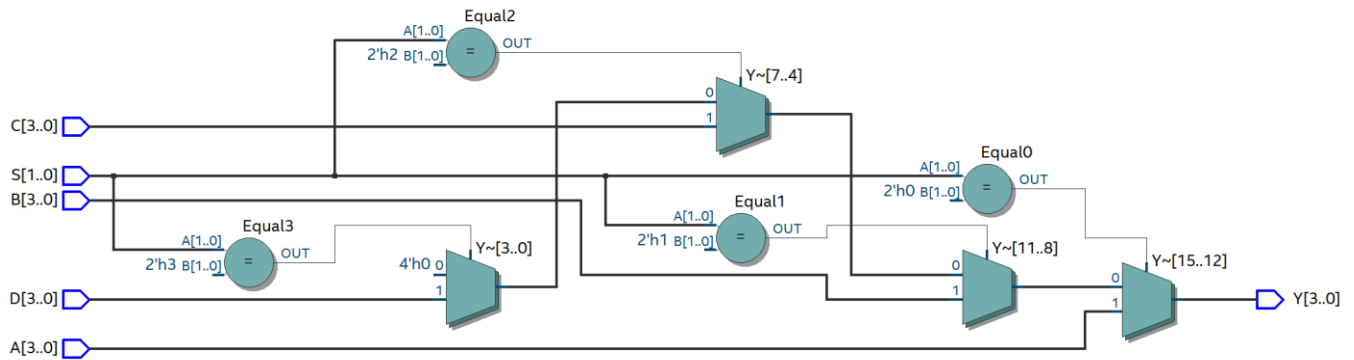


Figure 3.4 – 8-Bit 4x1 Line Multiplexer RTL Viewer

 


Figure 3.5 – I/O Ports