

Laboratory Report #5

Name: Paul Emmanuel G. Corsino

Date Completed: 17/11/2023

Laboratory Exercise Title: Behavioral Modeling of Combinational Circuits

Target Course Outcomes:

CO1: Create descriptions of digital hardware components such as in combinational and sequential circuits using synthesizable Verilog HDL constructs.

CO2: Verify the functionality of HDL-based components through design verification tools.

Exercise 5A:

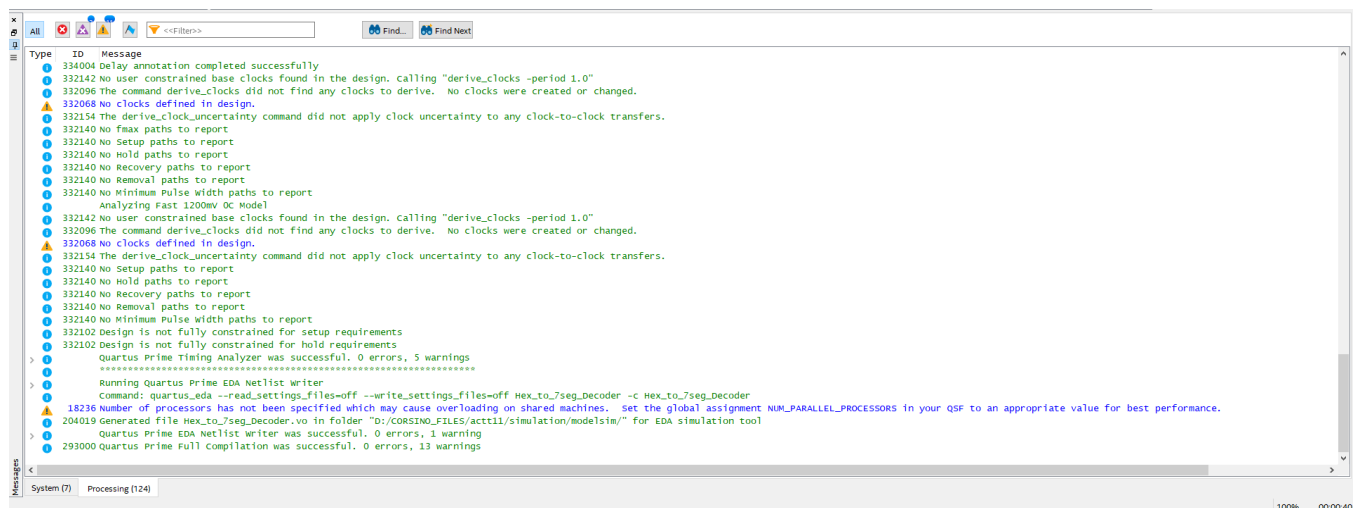


Figure 1. Proof of successful design synthesis

	Msgs	
/tb_Hex_to_7seg_Decoder/Hex	0000	0000 0001 0010 0011 0100 0101 0110 0111 1000 1001 1010 1011 1100 1101 1110 1111
/tb_Hex_to_7seg_Decoder/dp	1	
/tb_Hex_to_7seg_Decoder/S	11000000	1100... 0111... 1010... 0011... 0001... 1001... 1000... 0111... 1000... 0001... 1000... 0000... 0100... 1010... 1000... 0000...

Figure 2. Proof of successful simulation results

Explanation:

Given the input, 0000, it results in an output in the 7-segment showing 0, with 0 having "1111110" via Figure 4, as an output in the 7-segment to visualize the variable "0". It can be seen in Figure 2 that the S is valued "11000000" as the decimal point is turned on, while the following 8 bits is the alternate of the value of 0 via Figure 4. As 1 is 0 in S (in my wave), while the 1 bit in S is 0 to the value of bit in the truth table. Also, it is reversed from right to left, to left to right. Everything applies to the next set of waves. As my last wave's S value contains "00001110", and via the truth table, to display F, the 7 segment's value has to be "10001111".



Exercise 5B:

```

• 332140 No Hold paths to report
• 332140 No Recovery paths to report
• 332140 No Removal paths to report
• 332140 No Minimum Pulse Width paths to report
• Analyzing Fast 1200mV OC Model
• 332142 No user constrained base clocks found in the design. Calling "derive_clocks -period 1.0"
• 332096 The command derive_clocks did not find any clocks to derive. No clocks were created or changed.
▲ 332068 No clocks defined in design.
• 332154 The derive_clock_uncertainty command did not apply clock uncertainty to any clock-to-clock transfers.
• 332140 No Setup paths to report
• 332140 No Hold paths to report
• 332140 No Recovery paths to report
• 332140 No Removal paths to report
• 332140 No Minimum Pulse Width paths to report
• 332102 Design is not fully constrained for setup requirements
• 332102 Design is not fully constrained for hold requirements
• Quartus Prime Timing Analyzer was successful. 0 errors, 5 warnings
• *****
• Running Quartus Prime EDA Netlist Writer
• Command: quartus_eda --read_settings_files=off --write_settings_files=off ALU_nbit -c ALU_nbit
▲ 18236 Number of processors has not been specified which may cause overloading on shared machines. Set the global assignment NUM_PARALLEL_PROCESSORS in
• 204019 Generated file ALU_nbit.vo in folder "C:/School/HDL/LAB5-act2/simulation/modelsim/" for EDA simulation tool
• Quartus Prime EDA Netlist Writer was successful. 0 errors, 1 warning
• 293000 Quartus Prime Full Compilation was successful. 0 errors, 14 warnings

```

Figure 1. Proof of successful design synthesis

 


Figure 2. Proof of successful simulation results

Explanation:

```

# Initiating simulation at 0 ns.
# Time = 0 ns Mode = 000 A = 0100 B = 0010 CB_in = 1 Result = 0111 CB_out = 0
# Time = 10 ns Mode = 000 A = 1000 B = 1110 CB_in = 1 Result = 0111 CB_out = 1
# Time = 20 ns Mode = 000 A = 0101 B = 1100 CB_in = 0 Result = 0001 CB_out = 1
# Time = 30 ns Mode = 001 A = 0100 B = 0010 CB_in = 0 Result = 0010 CB_out = 0
# Time = 40 ns Mode = 001 A = 1000 B = 1110 CB_in = 0 Result = 1010 CB_out = 1
# Time = 50 ns Mode = 001 A = 0101 B = 1100 CB_in = 0 Result = 1001 CB_out = 1
# Time = 60 ns Mode = 010 A = 0100 B = 0010 CB_in = 0 Result = 0000 CB_out = 0
# Time = 70 ns Mode = 010 A = 1000 B = 1110 CB_in = 0 Result = 1000 CB_out = 0
# Time = 80 ns Mode = 010 A = 0101 B = 1100 CB_in = 0 Result = 0100 CB_out = 0
# Time = 90 ns Mode = 011 A = 0100 B = 0010 CB_in = 0 Result = 0110 CB_out = 0
# Time = 100 ns Mode = 011 A = 1000 B = 1110 CB_in = 0 Result = 1110 CB_out = 0
# Time = 110 ns Mode = 011 A = 0101 B = 1100 CB_in = 0 Result = 1101 CB_out = 0
# Time = 120 ns Mode = 100 A = 0100 B = 0010 CB_in = 0 Result = 0110 CB_out = 0
# Time = 130 ns Mode = 100 A = 1000 B = 1110 CB_in = 0 Result = 0110 CB_out = 0
# Time = 140 ns Mode = 100 A = 0101 B = 1100 CB_in = 0 Result = 1001 CB_out = 0
# Time = 150 ns Mode = 101 A = 1011 B = 1100 CB_in = 0 Result = 0100 CB_out = 0
# Time = 160 ns Mode = 101 A = 1000 B = 1100 CB_in = 0 Result = 0111 CB_out = 0
# Time = 170 ns Mode = 101 A = 0101 B = 1100 CB_in = 0 Result = 1010 CB_out = 0
# Time = 180 ns Mode = 110 A = 1011 B = 1100 CB_in = 0 Result = 1100 CB_out = 0
# Time = 190 ns Mode = 110 A = 1000 B = 1100 CB_in = 0 Result = 1001 CB_out = 0
# Time = 200 ns Mode = 110 A = 0101 B = 1100 CB_in = 0 Result = 0110 CB_out = 0
# Time = 210 ns Mode = 111 A = 1011 B = 1100 CB_in = 0 Result = 1010 CB_out = 0
# Time = 220 ns Mode = 111 A = 1000 B = 1100 CB_in = 0 Result = 0111 CB_out = 0
# Time = 230 ns Mode = 111 A = 0101 B = 1100 CB_in = 0 Result = 0100 CB_out = 0
# Simulation finished at 240 ns.
# ** Note: $stop : C:/School/HDL/LAB5-act2/tb_ALU_4bit.v(75)
# Time: 240 ns Iteration: 0 Instance: /tb_ALU_4bit

```

 


Figure 3. Proof of successful FPGA implementation